

TechNote Zig-zag Transformer

From OpenDSSWiki

How to Define a Zig-Zag Transformer

Here is a nice, compact script for modeling a zig-zag transformer courtesy of Bob Arritt:

```
New Transformer.ZZ1A phases=1 buses=[B1.1.5 B1.4.7] conns=[delta
delta] kVs=[16.4 16.4] kvas=[920.4 920.4] XHL=0.468
New Transformer.ZZ1B phases=1 buses=[B1.2.6 B1.4.5] conns=[delta
delta] kVs=[16.4 16.4] kvas=[920.4 920.4] XHL=0.468
New Transformer.ZZ1C phases=1 buses=[B1.3.7 B1.4.6] conns=[delta
delta] kVs=[16.4 16.4] kvas=[920.4 920.4] XHL=0.468

! ZZ1 Neutral
New Reactor.ZZ1 phases=1 bus1=B1.4 R=23.8 X=0 ! 0.001
```

In this script everything is connected to the same bus at different nodes. The main conductors are 1, 2, 3 and 4 (the neutral end). Nodes 5-7 are used for the internal connections. The transformer is to be applied to a 33 kV system. This the kV rating of each single phase winding is $(33/1.732) * 1.732/2$.

You can also do this by connecting the winding to different buses and then use short jumpers (LINE or REACTOR) to accomplish the connection. However, the definition shown works just fine and it is not necessary to use two buses.

Alternative

If only the zero sequence behavior need be modeled, and you are not serving any load off the zig-zag, you can get the same effect with a simple 2-winding Yg-D transformer.

For example, a definition that is equivalent to the one above in terms of zero sequence impedance is:

```
New Transformer.ZZ phases=3 buses=[B1.1.2.3.4 B1.5.6.7] conns=[Wye
delta] kVs=[33 16.4] kvas=[2761 2761] XHL=0.468

! ZZ1 Neutral
New Reactor.ZZ1 phases=1 bus1=B1.4 R=23.8 X=0 ! 0.001
```

The voltage rating of the delta winding is irrelevant.

--Rdugan 19:32, 26 July 2013 (UTC)

Retrieved from "http://localhost/mediawiki/index.php?title=TechNote_Zig-zag_Transformer&oldid=643"

- This page was last modified on 26 July 2013, at 11:32.
- This page has been accessed 156 times.